

## PHYSICS COURSE : US01CPHY02

### UNIT – 2 : BRIDGES AND THEIR APPLICATIONS


#### DC BRIDGES

#### INTRODUCTION

Bridges are used to measure the values of the electronic components. For example a Wheatstone Bridge is used to measure the unknown resistance of a resistor. However they are also used to measure the unknown inductance, capacitance, admittance, conductance or any of the impedance parameters.

Besides this bridge circuits are also used in the precision measurements in some circuits and for the interfacing of transducers. Actually nowadays fully automatic bridges which electronically null a bridge to make precision measurements are also used.

#### WHEATSTONE BRIDGE : BASIC OPERATION

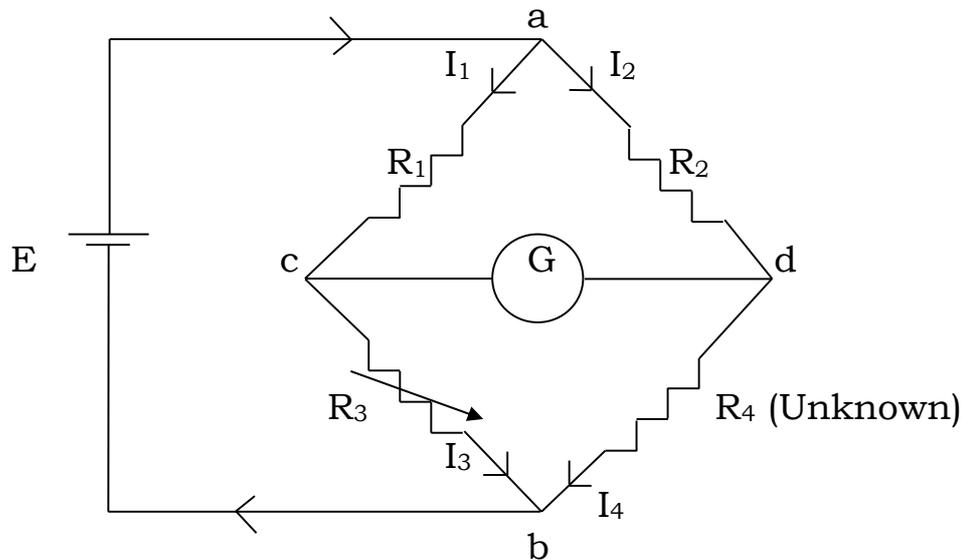

**Fig. (1)**

- The circuit diagram of Wheatstone Bridge is shown in Fig. (1). The four arms of the bridge  $ac$ ,  $ad$ ,  $cb$  and  $db$  contains the four resistors  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  respectively.  $G$  is a galvanometer or the null detector.  $E$  is the source of EMF.

- $I_1, I_2, I_3$  and  $I_4$  are the currents through the resistors  $R_1, R_2, R_3$  and  $R_4$ , respectively.
- When the current through galvanometer is zero, at that time terminals c and d are said to be at same potential with respect to point a i.e.,

$$E_{ac} = E_{ad} \quad (1)$$

- Hence the currents  $I_1 = I_3$  and  $I_2 = I_4$ . This is called the balance of the bridge. And for this condition, we can write,

$$I_1 R_1 = I_2 R_2 \quad (2)$$

Where

$$I_1 = I_3 = \frac{E}{R_1 + R_3} \quad (3)$$

and

$$I_2 = I_4 = \frac{E}{R_2 + R_4} \quad (4)$$

- Substituting the values of  $I_1$  and  $I_2$  from equations (3) and (4) into (2), we get

$$\frac{E}{R_1 + R_3} R_1 = \frac{E}{R_2 + R_4} R_2$$

$$\frac{R_1}{R_1 + R_3} = \frac{R_2}{R_2 + R_4}$$

therefore,  $R_1(R_2 + R_4) = R_2(R_1 + R_3)$

$$R_1 R_4 = R_2 R_3 \quad (5)$$

- Equation (5) is called the balance equation(condition) of the bridge. Here, if  $R_4$  is an unknown resistor, then its resistance  $R_x$  can be measured using the equation

$$R_1 R_x = R_2 R_3$$

$$R_x = \frac{R_2 R_3}{R_1} \quad (6)$$

- Here resistor  $R_3$  is called the standard arm, whereas  $R_2$  and  $R_1$  are called the ratio arms.

### **MEASUREMENT ERRORS (LIMITATIONS OF THE WHEATSTONE BRIDGE CIRCUIT OR SOURCES OF ERRORS IN WHEATSTONE BRIDGE MEASUREMENTS)**


- The major sources of errors in the Wheatstone bridge measurements are as follows :

- (1) Insufficient sensitivity of the null detector (galvanometer).
- (2) Heating effects of currents through the arm resistors : The currents flowing through the resistors produce heating effects in them and changes the resistance values. This affects the bridge balance. It leads to the  $I^2R$  losses in resistors. If an excess amount of current flows, the resistance values change permanently and this affects the subsequent measurements. This error becomes substantial particularly when low resistance values are to be measured. To avoid this, the current must be limited to a safe value.
- (3) Thermal EMF in the bridge circuit or the galvanometer circuit can also cause problems when low-value resistors are being measured. This limitation can be overcome using high sensitivity galvanometer having copper coil and copper suspension system in it.
- (4) Leads and Contacts : the resistance drops in the leads (wires) and contacts which are used in the external

bridge circuit affects the balance of bridge. This error can be minimized using a Kelvin bridge circuit.

### THEVENIN EQUIVALENT CIRCUIT (OF WHEATSTONE BRIDGE)

- With what accuracy a Wheatston bridge can be balanced depends upon the sensitivity of galvanometer.
- The amount of current per unit deflection is called the sensitivity of galvanometer.
- The balance of bridge is also affected by the internal resistance of galvanometer.
- The suitability of galvanometer for a particular bridge circuit can be known by using Thevenin equivalent circuit of that bridge.

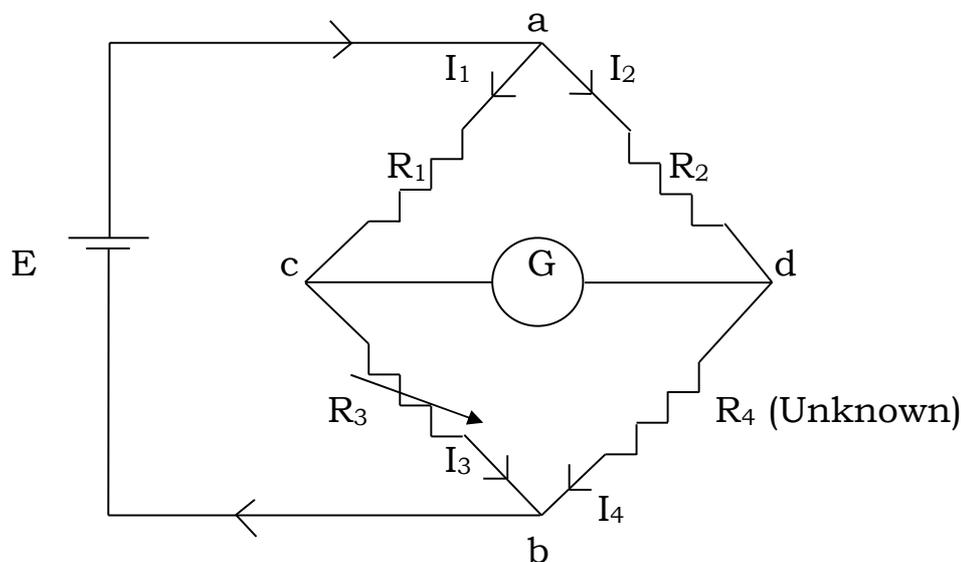

**Fig. (1)**

- Let us consider a Wheatston bridge circuit as shown in Fig. (1).
- When the bridge is balanced, points c and d are at the same potential with respect to point. Therefore, we can write

$$E_{cd} = E_{ac} - E_{ad} = I_1R_1 - I_2R_2 \quad (1)$$

- Also we can write currents  $I_1$  and  $I_2$  as


$$I_1 = I_3 = \frac{E}{R_1 + R_3} \quad (2)$$

$$\text{and } I_2 = I_4 = \frac{E}{R_2 + R_4} \quad (3)$$

- Then, substituting values of  $I_1$  and  $I_2$  from equations (2) and (3) into equation (1), we get

$$E_{cd} = E \left( \frac{R_1}{(R_1 + R_3)} - \frac{R_2}{(R_2 + R_4)} \right) \quad (4)$$

- In the circuit of Fig. (1) we can find the current through galvanometer by obtaining the Thevenin equivalent circuit of the bridge looking into the terminals c and d. This circuit is shown in Fig. (2).

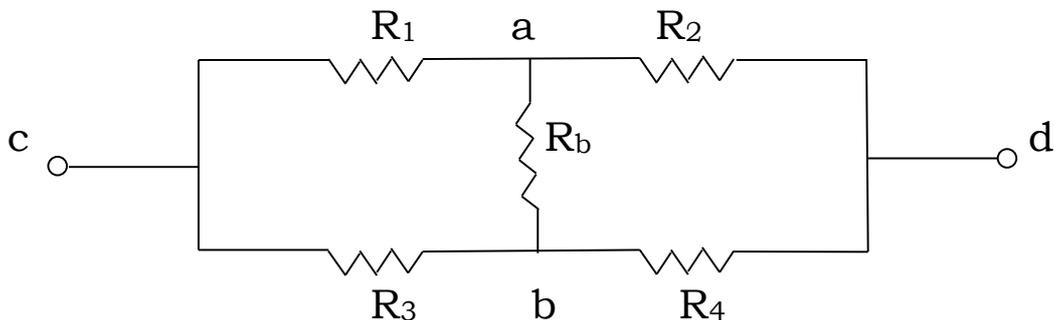

**Fig. (2)**


- The Thevenin Resistance, looking into the terminals c and d in Fig. (2) then becomes

$$R_{TH} = \left( \frac{R_1 R_3}{(R_1 + R_3)} + \frac{R_2 R_4}{(R_2 + R_4)} \right) \quad (5)$$

- The Thevenin equivalent voltage source  $E_{TH}$  is given by

$$E_{TH} = E_{cd}$$

- Now the Thevenin equivalent circuit can be shown as shown in Fig. (3) below.

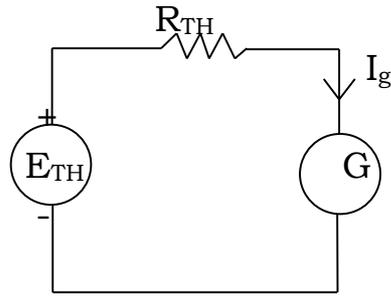

**Fig. (3)**

- Then the current through galvanometer is given by

$$I_g = \frac{E_{TH}}{R_{TH} + R_g} \quad (6)$$


Where  $R_g$  is the resistance of galvanometer.

### **LIMITATIONS OF WHEATSTONE BRIDGE**

- The Wheatstone bridge is limited to the measurement of resistances ranging from a few ohms to several megohms.
- The upper limit is set by the reduction in sensitivity of the bridge to unbalance condition, which is produced due to high resistance values of Thevenin equivalent resistance. This reduces the galvanometer current.
- The lower limit is set by the resistance of the connecting leads(wires/cables) and the contact resistances at the binding points. These resistances makes the measurements of low resistances difficult.
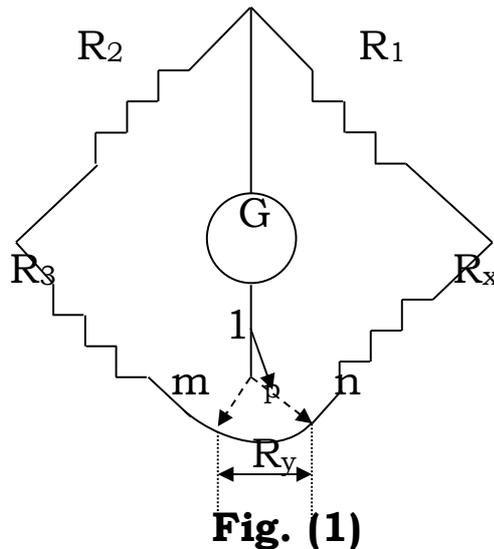
## KELVIN BRIDGE : EFFECTS OF CONNECTING LEADS

- The Kelvin bridge is the modification of Wheatstone bridge. It measures the low resistance values with more accuracy.
- Fig. (1) below shows the circuit diagram for the Kelvin bridge circuit.



- As shown in the Fig. (1) above  $R_y$  is the resistance of the connecting lead from  $R_3$  to  $R_x$ . Points m and n shows the two possible connections for galvanometer.
- When connection is made along 1n,  $R_y$  is added to  $R_3$  and when connection is made along 1m,  $R_y$  is added to  $R_x$ . However, when connection is made along 1p, resistance  $R_{np}$  is added to  $R_x$  and  $R_{mp}$  is added to  $R_3$ .
- The balancing condition demands that if the connection is along 1p, the ratio of resistance between n and p and between m and p, namely,  $R_{np}$  and  $R_{mp}$  respectively, will be given by

$$\frac{R_{np}}{R_{mp}} = \frac{R_1}{R_2} \quad (1)$$

$$\frac{R_{np} + R_{mp}}{R_{mp}} = \frac{R_1 + R_2}{R_2}$$

Therefore,  $R_{mp} = \frac{R_2 R_y}{R_1 + R_2}$  (2)

Similarly,  $R_{np} = \frac{R_1 R_y}{R_1 + R_2}$  (3)

- Now, the balance condition for the bridge becomes,

$$(R_x + R_{np})R_2 = R_1(R_3 + R_{mp})$$

$$R_x + R_{np} = \frac{R_1}{R_2}(R_3 + R_{mp})$$

- Then substituting the values of  $R_{np}$  and  $R_{mp}$  from equations (2) and (3) into the above equation, we get

$$R_x + \frac{R_1 R_y}{R_1 + R_2} = \frac{R_1}{R_2} \left( R_3 + \frac{R_2 R_y}{R_1 + R_2} \right)$$

$$R_x + \frac{R_1 R_y}{R_1 + R_2} = \frac{R_1 R_3}{R_2} + \frac{R_1 R_y}{R_1 + R_2}$$


$$R_x = \frac{R_1 R_3}{R_2} \quad (4)$$

- Equation (4) above is called the balance equation and it shows that the effect of resistance of the connecting lead from m to n has been removed by connecting the galvanometer to the intermediate position p.

## AC BRIDGES AND THEIR APPLICATIONS

### CONDITIONS FOR BRIDGE BALANCE

- An ac bridge consists of four bridge arms, a source of excitation and a null detector. The power source is an ac source and the null detector is usually a headphone.
- An ac bridge having impedances  $Z_1$ ,  $Z_2$ ,  $Z_3$  and  $Z_4$  in its arms is shown in the Fig. (1) below.

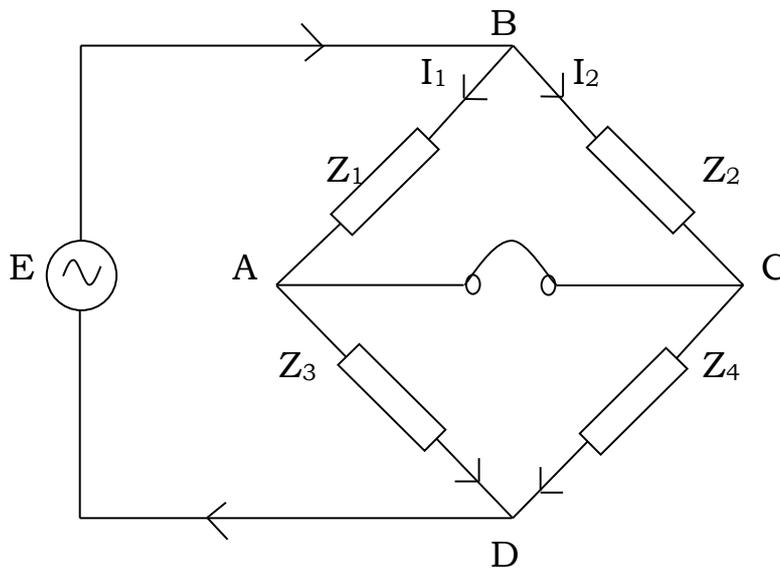

**Fig. (1)**

- When balance of the bridge is obtained the terminals A and C are said to be at same potential with respect to point B i.e.,

$$E_{AB} = E_{BC} \quad (1)$$

- For this condition, we can write,

$$I_1 Z_1 = I_2 Z_2 \quad (2)$$

Where

$$I_1 = \frac{E}{Z_1 + Z_3} \quad (3)$$

and

$$I_2 = \frac{E}{Z_2+Z_4} \quad (4)$$

• Substituting the values of  $I_1$  and  $I_2$  from equations (3) and (4) into (2), we get

$$\frac{E}{Z_1+Z_3} Z_1 = \frac{E}{Z_2+Z_4} Z_2$$

$$\frac{Z_1}{Z_1+Z_3} = \frac{Z_2}{Z_2+Z_4}$$

therefore,  $Z_1(Z_2+Z_4) = Z_2(Z_1+Z_3)$

$$Z_1 Z_4 = Z_2 Z_3 \quad (5)$$

• Equation (5) is called the general equation for balance of ac bridge. Similarly, we can also write this equation in terms of admittances( $Y$ ) instead of impedences as

$$Y_1 Y_4 = Y_2 Y_3 \quad (6)$$

• If the impedance is written in the form of  $Z = \underline{Z} \theta$  , then equation (5) can be written as

$$(Z_1/\theta_1) (Z_4/\theta_4) = (Z_2/\theta_2) (Z_3/\theta_3)$$

$$Z_1 Z_4 / (\theta_1 + \theta_4) = Z_2 Z_3 / (\theta_2 + \theta_3) \quad (7)$$

• Equation (7) shows two balance conditions. The first condition is that the magnitudes of the impedances satisfy the relationship shown by equation (5).

• It states that “The products of the magnitudes of impedances of the opposite arms must be equal”.


• The second condition requires that the phase angles of the impedances satisfy the relationship

$$\underline{\theta}_1 + \underline{\theta}_4 = \underline{\theta}_2 + \underline{\theta}_3 \quad (8)$$

• It states that “The sum of the phase angles of the opposite arms must be equal”.

## MAXWELL BRIDGE

- The Maxwell bridge is used to measure an unknown inductance in terms of a known capacitance. The circuit for the Maxwell Bridge is shown in Fig. (1) below.

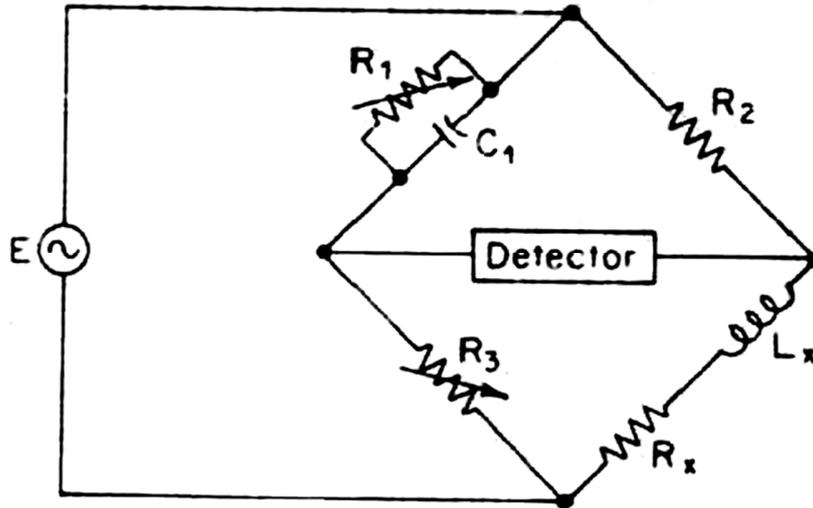

**Fig. (1)**

- As shown in Fig. (1), the ratio arm has parallel combination of resistance  $R_1$  and a capacitance  $C_1$ .
- The unknown arm contains unknown inductance  $L_x$  and resistance  $R_x$ .
- The balance condition of the bridge can be given by

$$Z_1 Z_X = Z_2 Z_3$$

$$Z_X = Z_2 Z_3 Y_1 \quad (1)$$

where  $Y_1 = 1/Z_1 = \text{admittance}$

- The bridge is balanced by first adjusting  $R_3$  for inductive balance and then by adjusting  $R_1$  for resistive balance.
- Adjustment of  $R_1$  disturbs the inductive balance and  $R_3$  needs to be modified and accordingly  $R_1$  also is modified.

- The process gives a slow convergence and the balance slowly shifts towards the actual null point. This type of balance is called the ‘sliding balance’. The actual null point is obtained after few adjustments.
- From Fig. (1) we can write the impedance of the arms as

$$Y_1 = \frac{1}{Z_1} = \frac{1}{R_1} + \frac{j}{X_1} = \frac{1}{R_1} + j\omega C_1 \quad (2)$$

$$Z_2 = R_2 ; \quad Z_3 = R_3 \quad (3)$$

$$Z_x = R_x + jX_L = R_x + j\omega L_x \quad (4)$$

$$R_x + j\omega L_x = R_2 R_3 \left( \frac{1}{R_1} + j\omega C_1 \right)$$

$$R_x + j\omega L_x = \left( \frac{R_2 R_3}{R_1} + j\omega C_1 R_1 R_2 \right)$$

- Equating the real parts of the above equation we get


$$R_x = \frac{R_2 R_3}{R_1}$$

- Equating the imaginary parts we get

$$L_x = R_2 R_3 C_1$$

- **Limitation of the Maxwell bridge** is that it is not suitable for the determination of the self-inductance of coils having quality factor  $Q > 10$  or  $Q < 1$ . It is suitable for the coils having  $Q$  values in the range  $1 < Q < 10$ .
- This is because for high  $Q$  coils the phase angle is very nearly  $90^\circ$  (positive). This requires a capacitor having phase angle very nearly equal to  $90^\circ$  (positive).
- This situation demands that  $R_1$  should be very large, which is impractical.

## HAY BRIDGE

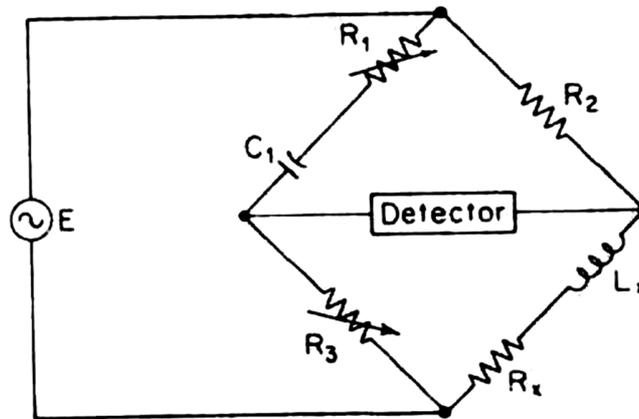

**Fig. (1)**

- Hay bridge is usually used to determine the unknown inductance of coils having higher Q values(>10).
- It consists of resistor  $R_1$  in series with standard capacitor  $C_1$  as shown in Fig. (1).
- The balance condition for the bridge is given by

$$Z_1 Z_x = Z_2 Z_3 \quad (1)$$

- The impedances of the arms of the bridge can be given by

$$Z_1 = R_1 - jX_{C1} = R_1 - \frac{j}{\omega C_1} ; \quad Z_2 = R_2 ; \quad Z_3 = R_3 ; \quad (2)$$

$$Z_x = R_x + jX_{Lx} = R_x + j\omega L_x \quad (3)$$

- Substituting the values from equations (2) and (3) into equation (1), we get

$$\left( R_1 - \frac{j}{\omega C_1} \right) (R_x + j\omega L_x) = R_2 R_3$$

It can be expanded as

$$R_1 R_x + \frac{L_x}{C_1} - \frac{jR_x}{\omega C_1} + j\omega L_x R_1 = R_2 R_3 \quad (4)$$

- Separating the real and imaginary terms on both the sides of equation (4) we get

$$R_1 R_x + \frac{L_x}{C_1} = R_2 R_3 \quad (5)$$

$$-\frac{jR_x}{\omega C_1} + j\omega L_x R_1 = 0$$


$$\frac{jR_x}{\omega C_1} = j\omega L_x R_1 \quad \text{or} \quad \frac{R_x}{\omega C_1} = \omega L_x R_1 \quad (6)$$

- Here both equations (5) and (6) contain  $L_x$  and  $R_x$  and to find their values we must solve them. The solution gives the following values of  $L_x$  and  $R_x$ .

$$R_x = \frac{\omega^2 C_1^2 R_1 R_2 R_3}{1 + \omega^2 C_1^2 R_1^2} \quad (7)$$

And 
$$L_x = \frac{R_2 R_3 C_1}{1 + \omega^2 C_1^2 R_1^2} \quad (8)$$

- Now the impedance triangles for the inductive and capacitive arms can be represented as in Fig. (2).

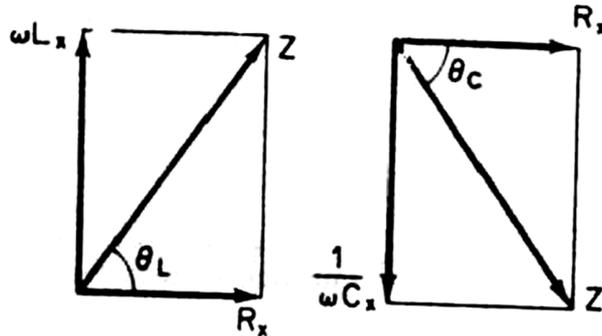

**Fig. (2)**

- In Fig. (2)  $\theta_L$  and  $\theta_C$  are the inductive and capacitive phase angles respectively. Then from the Fig. we can write

$$\tan \theta_L = \frac{X_L}{R} = \frac{\omega L_x}{R_x} = Q$$

$$\text{and } \tan \theta_C = \frac{X_C}{R} = \frac{1}{\omega C_1 R_1}$$

- When the two phase angles are equal, we have

$$\tan \theta_L = \tan \theta_C$$

$$Q = \frac{1}{\omega C_1 R_1} \tag{9}$$

- Then  $L_x$  can be given by the equation

$$L_x = \frac{R_2 R_3 C_1}{1 + \left(\frac{1}{Q}\right)^2}$$


- So for  $Q > 10$ ,  $(1/100) \ll 1$  and hence we have

$$L_x = R_2 R_3 C_1$$

- Thus for  $Q > 10$  Hay bridge is the most suitable bridge, however, for  $Q < 10$ ,  $(1/Q)^2$  is not negligible and hence Maxwell bridge is more suitable.

## SCHERRING BRIDGE

- A Scherring Bridge is generally used to determine the unknown capacitance of a capacitor. However, it is sometimes also used to measure the insulating or dielectric properties of materials.
- The circuit arrangements for the bridge are given below in Fig. (1).

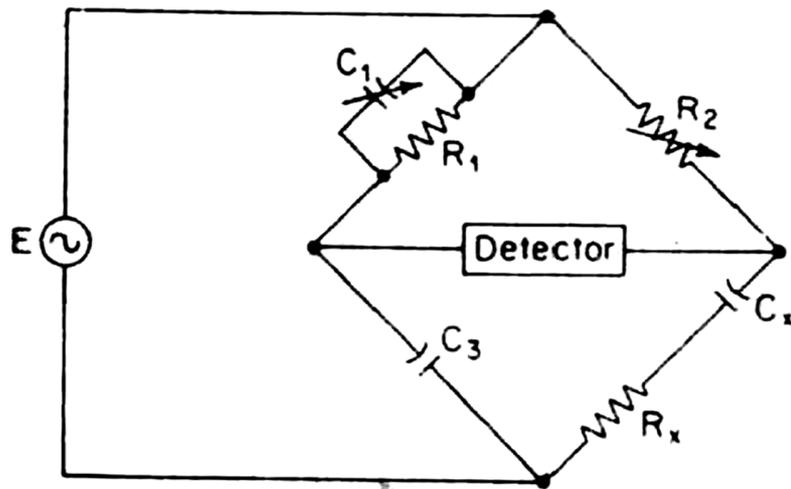

**Fig. (1)**

- Here, the ratio arm has the capacitor  $C_1$  in parallel with resistor  $R_1$ .
- The balance condition for the bridge is given by the equation

$$Z_x = Z_2 Z_3 Y_1 \quad (1)$$

- The impedances of the arms are given by

$$\frac{1}{Z_1} = Y_1 = \frac{1}{R_1} + \frac{j}{X_{C1}} = \frac{1}{R_1} + j\omega C_1 \quad ; \quad Z_2 = R_2 \quad ; \quad (2)$$

$$Z_3 = -jX_{C3} = \frac{-j}{\omega C_3} \quad ; \quad Z_x = R_x - jX_{Cx} = R_x - \frac{j}{\omega C_x} \quad (3)$$

- Substituting the values from equations (2) and (3) into equation (1), we get

$$R_x - \frac{j}{\omega C_x} = R_2 \left( \frac{-j}{\omega C_x} \right) \left( \frac{1}{R_1} + j\omega C_1 \right)$$

$$R_x - \frac{j}{\omega C_x} = \frac{R_2 C_1}{C_3} - \frac{j R_2}{\omega C_3 R_1}$$

- Then equating the real and imaginary parts in the above equation, we get

$$R_x = R_2 C_1 / C_3 \quad \text{and} \quad C_x = C_3 R_1 / R_2 \quad (4)$$

- The power factor for the series RC combination is defined as the cosine of the phase angle of the circuit. It is given by

$$\text{PF} = R_x / X_x = \omega C_x R_x \quad (5)$$

- Similarly, the dissipation factor of a series RC circuit is defined as the cotangent of the phase angle of the circuit. It is given by

$$D = \omega C_1 R_1 \quad (6)$$

## WIEN BRIDGE

- A Wien bridge is generally used to measure the frequency of the source. It is also extensively used in other applications like, harmonic distortion analyser, in audio and HF oscillators as the frequency determining element, etc.

- As shown in Fig. (1) below, the Wien bridge consists of a series RC combination in one arm and a parallel RC combination in the adjoining arm.

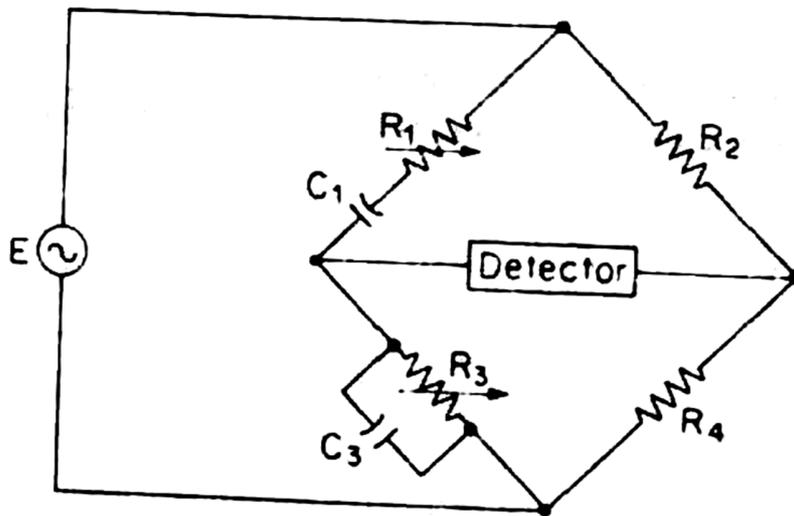


Fig. (1)

- The balance condition for the bridge is given by

$$Z_2 Z_3 = Z_1 Z_4$$

$$Z_2 = Z_1 Z_4 (1/Z_3) = Z_1 Z_4 Y_3 \quad (1)$$

- Now the impedances of the arms are given by the following equations

$$Z_1 = R_1 - jX_{C1} = R_1 - \frac{j}{\omega C_1} \quad ; \quad Z_2 = R_2 \quad (2)$$

$$1/Z_3 = Y_3 = \frac{1}{R_3} + \frac{j}{X_{C3}} = \frac{1}{R_3} + j\omega C_3 \quad ; \quad Z_4 = R_4 \quad (3)$$

- Substituting the values from equations (2) and (3) into equation (1), we get

$$R_2 = \left( R_1 - \frac{j}{\omega C_1} \right) R_4 \left( \frac{1}{R_3} + j\omega C_3 \right)$$

$$R_2 = \frac{R_1 R_4}{R_3} + j\omega C_3 R_1 R_4 - \frac{jR_4}{\omega C_1 R_3} + \frac{R_4 C_3}{C_1} \quad (4)$$

- Equating the real parts we get,

$$R_2 = \frac{R_1 R_4}{R_3} + \frac{R_4 C_3}{C_1}$$

- Dividing by  $R_4$  on both the sides we get

$$\frac{R_2}{R_4} = \frac{R_1}{R_3} + \frac{C_3}{C_1} \quad (5)$$

- Now equating the imaginary parts we get,

$$j\omega C_3 R_1 R_4 = \frac{jR_4}{\omega C_1 R_3} \quad (6)$$

$$\omega^2 = \frac{1}{C_1 C_3 R_1 R_3} \quad \text{where } \omega = 2\pi f$$

$$f = \frac{1}{2\pi\sqrt{C_1 C_3 R_1 R_3}} \quad (7)$$

- If  $R_1 = R_3 = R$  and  $C_1 = C_3 = C$ , then we get  $R_2 = 2R_4$  and

$$f = \frac{1}{2\pi RC} \quad (8)$$

- Using the above equation, we can determine the frequency of the source. Also the bridge can be calibrated directly in terms of frequency.

## MULTIPLE CHOICE QUESTIONS

- How many arms does a Wheatstone bridge possess?  
(a) one (b) two **(c) four** (d) three
- When a Wheatstone bridge is balanced ideally the current through the galvanometer should be  
**(a) 0 A** (b) 1 A (c) 1.5 A (d) 2 A
- Wheatstone bridge is used to find unknown  
**(a) resistance** (b) reactance (c) inductance (d) capacitance
- In an ac bridge the null detector is usually  
(a) a galvanometer (b) an ammeter  
**(c) a head phone** (d) a voltmeter
- The inductive reactance of a coil( $X_L$ ) is given by the following equation  
(a)  $X_L = (1/2\pi)fL$  (b)  $X_L = 2\pi/(fL)$  **(c)  $X_L = 2\pi fL$**  (d)  $X_L = 2\pi f/L$
- The capacitive reactance of a capacitor ( $X_C$ ) is given by the following equation  
(a)  $X_C = 1/fC$  **(b)  $X_C = 1/(2\pi fC)$**  (c)  $X_C = 2\pi/fC$  (d)  $X_C = 2\pi f/C$
- Maxwell bridge is generally used to measure the unknown  
(a) resistance (b) reactance **(c) inductance** (d) capacitance
- Maxwell bridge is suitable for the coils having Quality factor in the range  
(a)  $0.1 < Q < 1$  **(b)  $1 < Q < 10$**  (c)  $0.01 < Q < 0.1$  (d)  $10 < Q < 1$
- Hay bridge is suitable for the coils having Quality factor  
**(a)  $Q > 10$**  (b)  $Q < 10$  (c)  $Q = 10$  (d)  $Q < 1$

10. Scherring bridge is used to determine the unknown  
(a) resistance (b) reactance (c) inductance **(d) capacitance**
11. Wien bridge is used to measure the unknown  
(a) resistance (b) reactance **(c) frequency** (d) capacitance
12. When the balance condition is satisfied in an ac bridge the ratio of \_\_\_\_\_ of the adjoining arms are equal.  
(a) resistances **(b) impedances** (c) reactances (d) phase angles
13. When the balance condition is satisfied in an ac bridge the sum of the \_\_\_\_\_ of the opposite arms are equal.  
(a) resistances (b) impedances (c) reactances **(d) phase angles**
14. When the balance condition is satisfied in an dc bridge the ratio of the \_\_\_\_\_ of the adjoining arms are equal.  
**(a) resistances** (b) impedances (c) reactances (d) phase angles
15. An inductor offers a \_\_\_\_ resistance to the high frequency current flowing through it.  
(a) low (b) zero **(c) high** (d) infinite
16. A capacitor offers a \_\_\_\_ resistance to the high frequency current flowing through it.  
**(a) low** (b) zero (c) high (d) infinite

### **SHORT QUESTIONS : (TWO MARKS)**

1. Draw the circuit diagram for the Wheatstone Bridge and write its balance condition.
2. Write the balance conditions for an ac bridge.
3. Enlist the possible sources of errors in the Wheatstone bridge measurement.
4. Explain the effect of heating of resistors and the thermo-emf on the Wheatstone bridge measurements.

5. Explain the effect of leads and contacts and the thermo-emf on the Wheatstone bridge measurements.
6. Write a note on limitations of Wheatstone bridge.
7. Discuss the limitations of Maxwell bridge.

### **LONG QUESTIONS**

1. Discuss the basic operation of a Wheatstone bridge and derive its balance condition. **(4)**
2. Discuss in detail the various sources of errors associated with the Wheatstone bridge measurements. **(4)**
3. Obtain the Thevenin equivalent circuit of a Wheatstone bridge and hence derive the formula for the current flowing through the galvanometer. **(6)**
4. With the help of necessary circuit diagram and equations explain how Kelvin bridge is used to account for the errors introduced due to the leads and contacts. **(4)**
5. Derive the balance condition for an ac bridge with the help of the necessary circuit diagram. **(4)**
6. Describe the construction and working of Maxwell bridge and discuss the procedure to determine the unknown inductance of a coil using it. Also explain its limitations. **(7)**
7. Discuss the Hay bridge circuit in detail and explain how it overcomes the drawbacks of Maxwell bridge circuit in determining the unknown inductances. **(7)**
8. Explain the construction and working of a Scherring bridge in detail. **(5)**
9. Explain the construction and working of a Wien bridge in detail. **(5)**